

ALU Construction

(ALU)

Arithmetic Logic Unit



does computation:

- add, sub.
- or, and (logical)
- register comparison for branches
- address computation for memory instructions

Steps

1. Pick operations to support.
2. Design a 1-bit ALU.



Decide which operations to support

Operation	OpCode
AND	00
OR	01
Add	10
Sub	11

- Choose operations
- Assign op-codes

Design 1-bit for each operation

And & Or

  

Design 1-bit for each operation



inputs		outputs		
A	B	Cin	Cout	Out
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Add


$$C_{out} = (A \cdot B) + (B \cdot C_{in}) + (A \cdot C_{in})$$

\uparrow AND \uparrow OR
  
$$Out = A \text{ XOR } B \text{ XOR } C_{in}$$



0111
+ 0011

 

A + B


Design 1-bit for each operation

Sub

subtract


$$A - B$$
$$A + (-B)$$

*1. flip bits
2. add 1*


 


0110
- 0011 →


Use MUX to choose between results

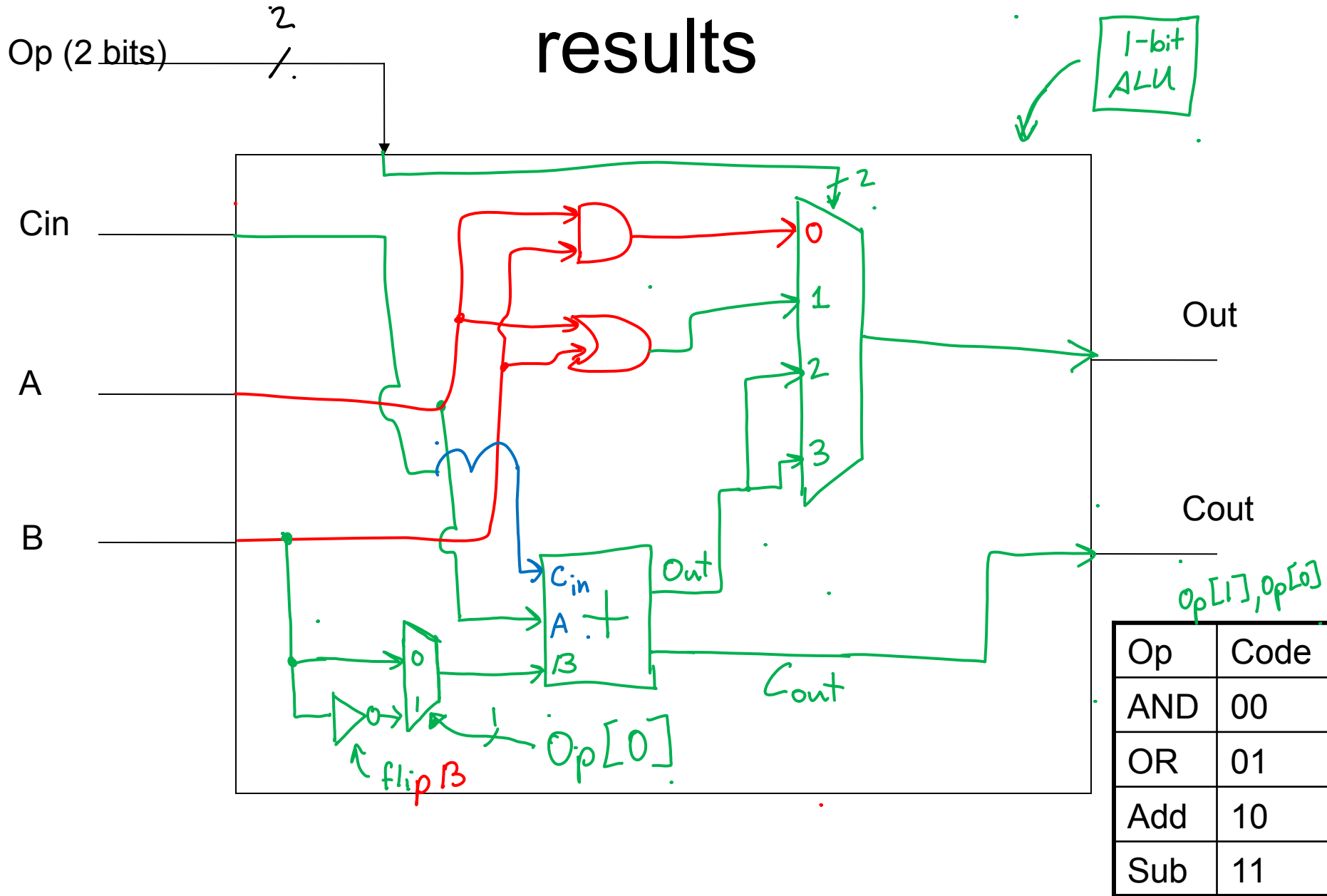

Design logic to connect ALU

  

Ripple Carry Adder

 

Adder Design

Problem: *Ripple Carry adder is slow.*

Solution: *compute carry information as quickly as possible.*

Carry Look-ahead (CLA)

We already know:



$$C_{i+1} = \overline{a_i} \cdot b_i + \overline{a_i} \cdot c_i + \overline{b_i} \cdot c_i$$

$$= \underbrace{a_i \cdot b_i}_{G_i} + c_i \cdot \underbrace{(a_i + b_i)}_{P_i}$$

$$= G_i + c_i \cdot P_i$$


generate
(this alu will generate a carry)

  propagate
(this alu will propagate a carry in)



- G_i and P_i can be computed in parallel

Carry Look-Ahead

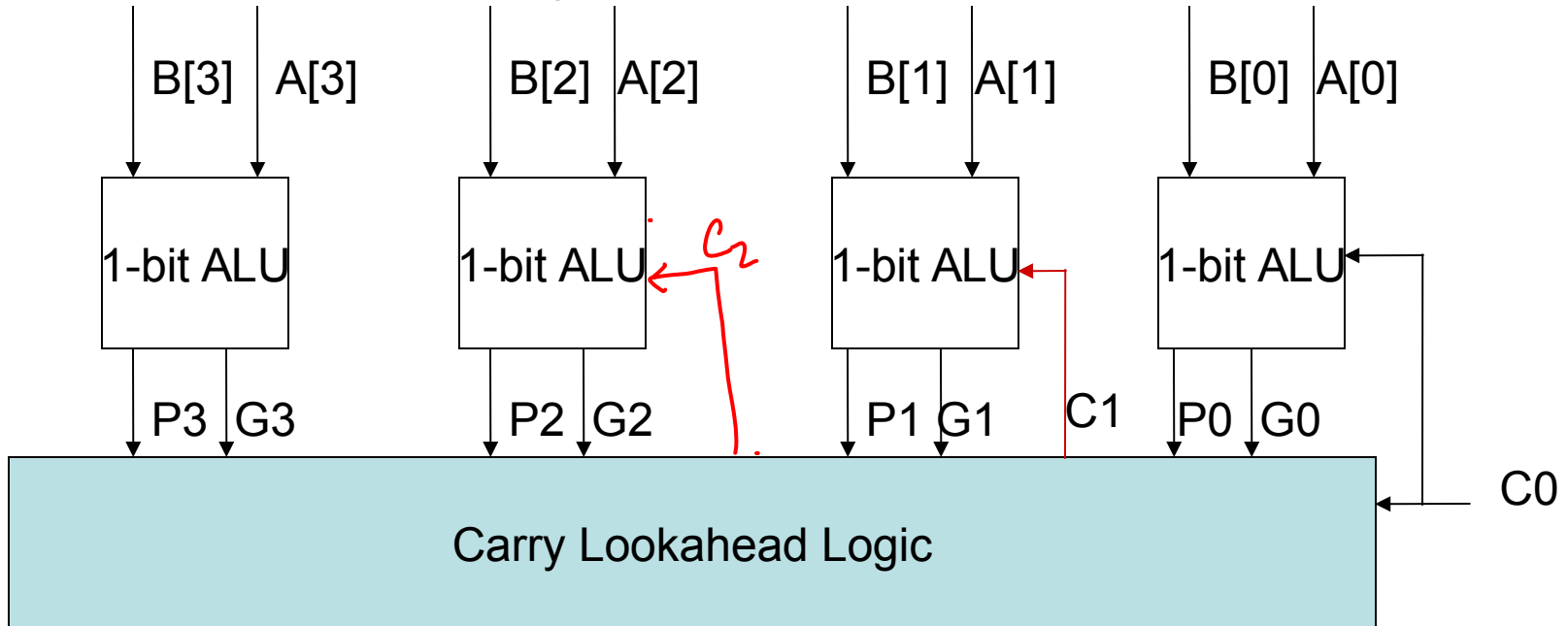

$$C_1 = G_0 + C_0 \cdot P_0$$


$$C_2 = G_1 + C_1 \cdot P_1$$

$$= G_1 + (G_0 + C_0 \cdot P_0) \cdot P_1$$


$$= G_1 + G_0 \cdot P_1 + C_0 \cdot P_0 \cdot P_1$$

OR

Why is it faster?

 

16-bit CLA Adder

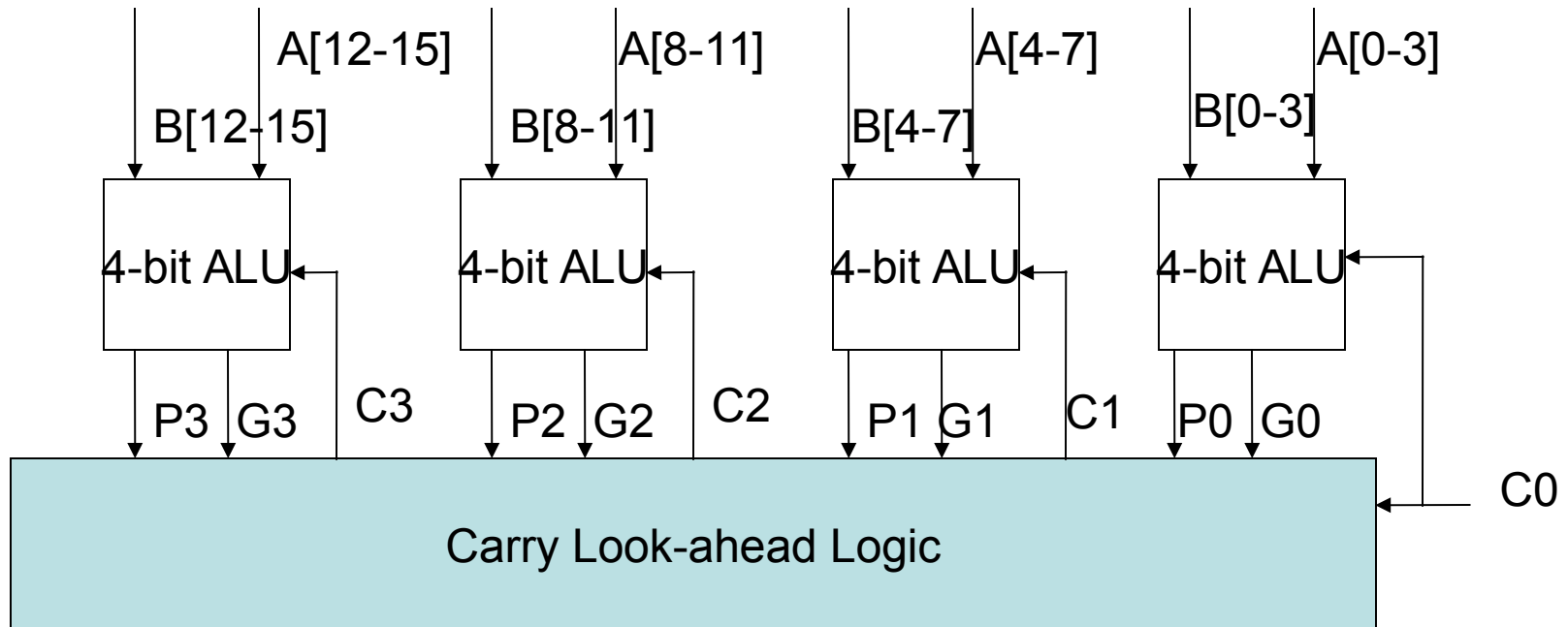

Carry Select
Adder.

